

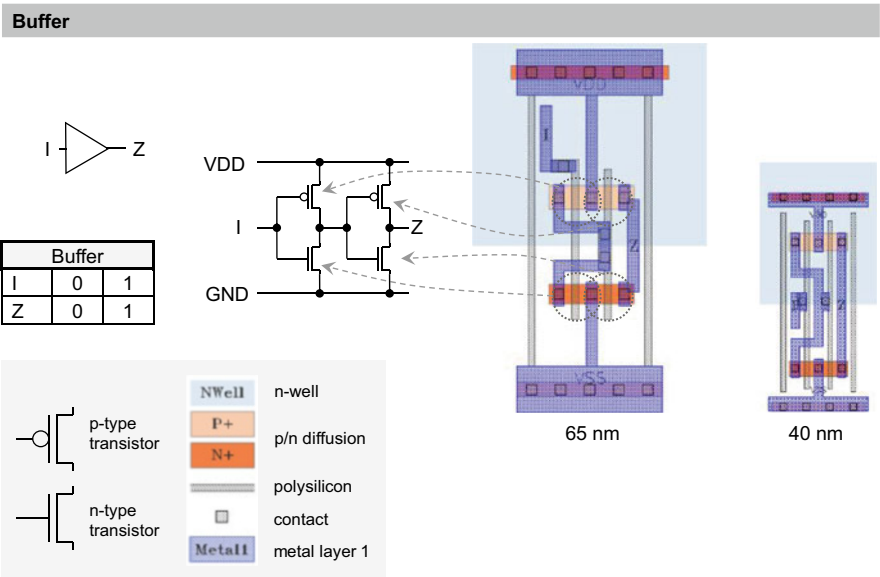




### 9.3 Example CMOS Cell Layouts

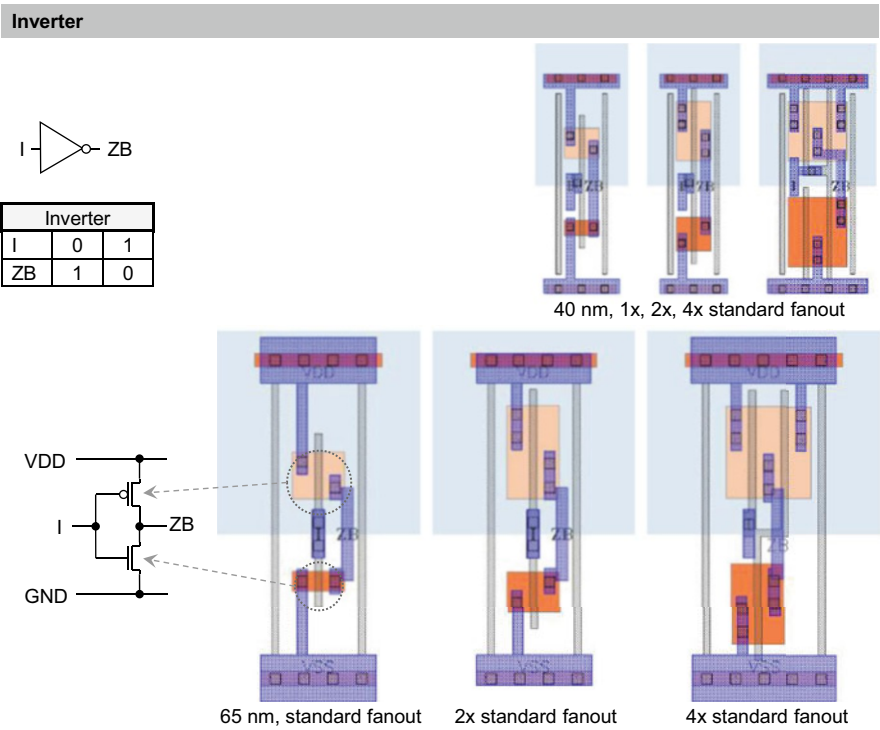


## NAND gate (2-input)

 


NAND				
A1	0	0	1	1
A2	0	1	0	1
ZB	1	1	1	0

  

65 nm, standard fanout

 


40 nm, 1x and 2x standard fanout


 


65 nm, 2x standard fanout


## NOR gate (2-input)

 


NOR				
A1	0	0	1	1
A2	0	1	0	1
ZB	1	0	0	0

  

65 nm, standard fanout

 


40 nm, 1x and 2x standard fanout

 


65 nm, 2x standard fanout


**AND-OR-Invert (AOI) gate (2-1)**

 


AOI								
A	0	0	0	0	1	1	1	1
B1	0	0	1	1	0	0	1	1
B2	0	1	0	1	0	1	0	1
ZB	1	1	1	0	0	0	0	0

 

40 nm, 1x and 2x standard fanout

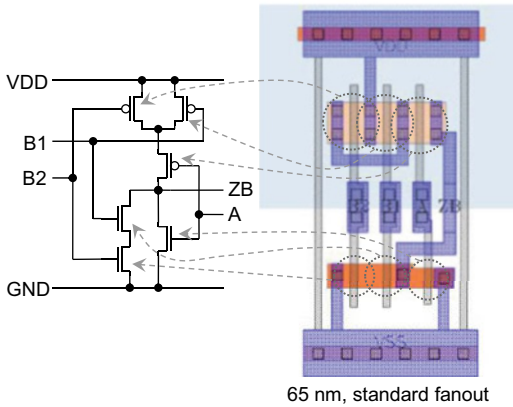

65 nm, standard fanout

 

65 nm, 2x standard fanout

